

HOMEWORK #2

EE 119a

Adam Krivk

- helper variable for the block of 1s for the delimiters

$VD, S, G:$

$$I_4 I_6 +$$
$$I_3(I_1 + I_5)$$
[illegible]

- $V0 = I_0 + I_3$

- $V1 = I_5$

↙ helper variable for the block of 1s for the delimiters

- $VD = \bar{I}_0 \bar{I}_1 \bar{I}_5 \bar{I}_6 + I_0 \bar{I}_1 I_2 + I_4 I_6$

- $V2 = I_6 + VD$

- $V3 = I_4 + I_3 \bar{I}_6 + VD$

↑ this term can be omitted in both V2 and V3 because $I_4 + I_4 I_6 = I_4$ and $I_6 + I_4 I_6 = I_6$

- $S = \bar{I}_3 (I_1 + I_5)$

- $G = \bar{I}_4 \bar{I}_5 \bar{I}_6 (\bar{I}_0 I_2 I_3 + \bar{I}_0 \bar{I}_1 I_2 + I_0 \bar{I}_2 I_3 + I_0 I_1 \bar{I}_2) +$

$$+ \bar{I}_4 \bar{I}_5 I_6 (\bar{I}_0 \bar{I}_2 I_3 + \bar{I}_0 I_1 \bar{I}_2 + I_0 \bar{I}_1 I_2 \bar{I}_3) +$$

$$+ \bar{I}_0 \bar{I}_1 \bar{I}_2 \bar{I}_3 I_4 I_5 \bar{I}_6 +$$


$$+ \bar{I}_4 I_5 \bar{I}_6 (\bar{I}_0 \bar{I}_1 I_2 \bar{I}_3 + I_0 \bar{I}_1 \bar{I}_2) +$$

$$+ \bar{I}_4 \bar{I}_5 I_6 (\bar{I}_0 \bar{I}_1 \bar{I}_2 I_3 + \bar{I}_0 I_1 \bar{I}_2 \bar{I}_3 + I_0 \bar{I}_1 I_2 \bar{I}_3) +$$

$$+ I_4 \bar{I}_5 I_6 (\bar{I}_0 \bar{I}_1 I_2 \bar{I}_3 + I_0 \bar{I}_1 \bar{I}_2 I_3) +$$


$$+ \bar{I}_0 \bar{I}_1 \bar{I}_2 \bar{I}_3 \bar{I}_4 I_5 I_6$$

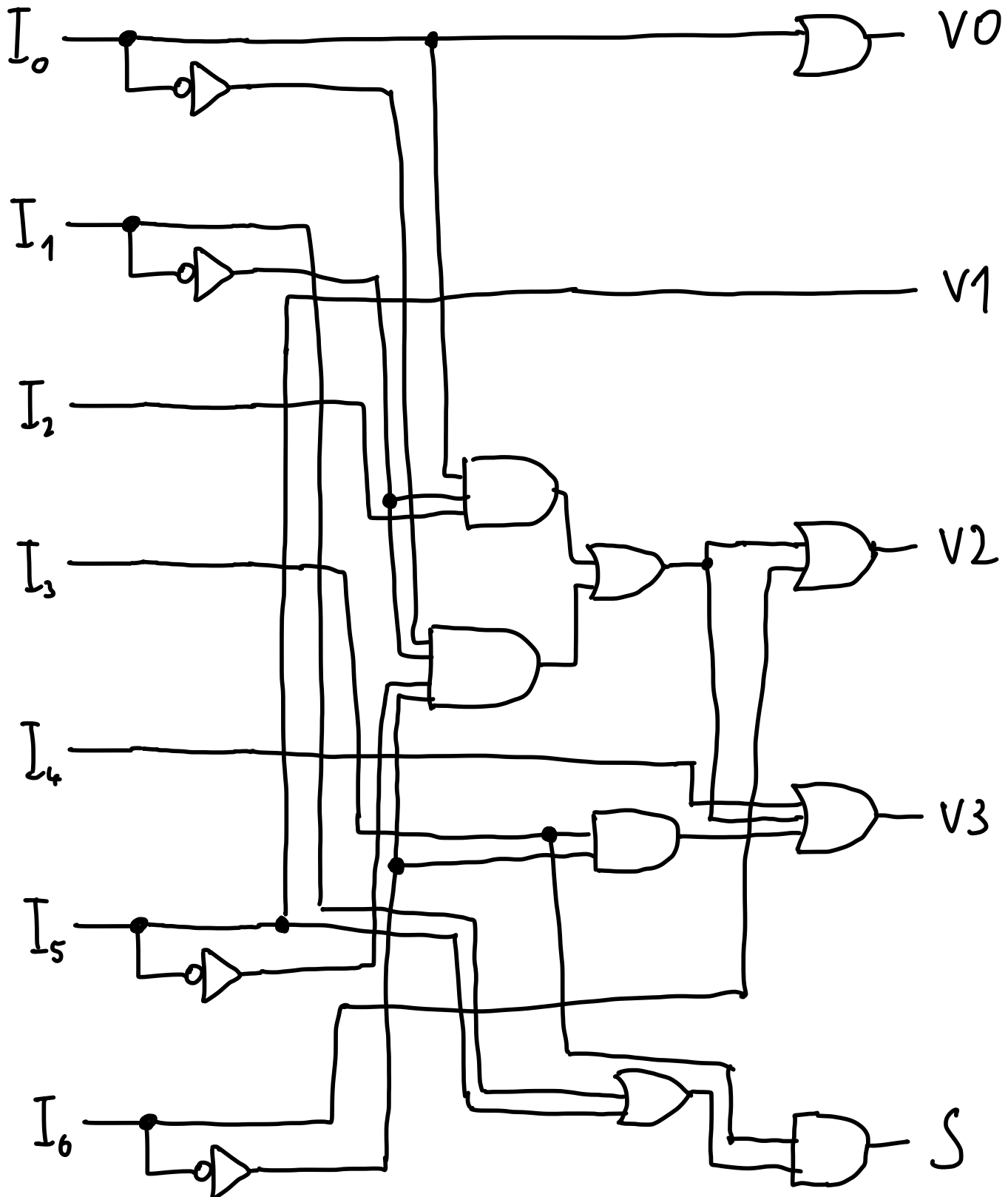I'll draw logic diagrams for $\{V_0, V_1, V_2, V_3, S\}$ and $\{G\}$ separately.



An even more simplified expression for G using XORs (shared terms are highlighted):


$$\begin{aligned}
 G = & \bar{I}_4 \bar{I}_5 \bar{I}_6 (\bar{I}_1 + I_3) (\bar{I}_0 \# I_2) + \\
 & + \bar{I}_4 \bar{I}_5 I_6 (\bar{I}_0 \bar{I}_2 (\bar{I}_1 + I_3) + I_0 \bar{I}_1 I_2 \bar{I}_3) + \\
 & + I_4 \bar{I}_5 I_6 \bar{I}_1 I_3 (\bar{I}_0 \# I_2) + \\
 & + \bar{I}_4 I_5 \bar{I}_6 \bar{I}_1 (\bar{I}_0 I_2 \bar{I}_3 + I_0 \bar{I}_2) + \\
 & + \bar{I}_0 \bar{I}_1 \bar{I}_2 \bar{I}_3 I_5 (I_4 \# I_6) + \\
 & + \bar{I}_4 \bar{I}_5 I_6 (\bar{I}_0 \bar{I}_1 \bar{I}_2 I_3 + \bar{I}_0 I_1 \bar{I}_2 \bar{I}_3 + I_0 \bar{I}_1 I_2 \bar{I}_3)
 \end{aligned}$$

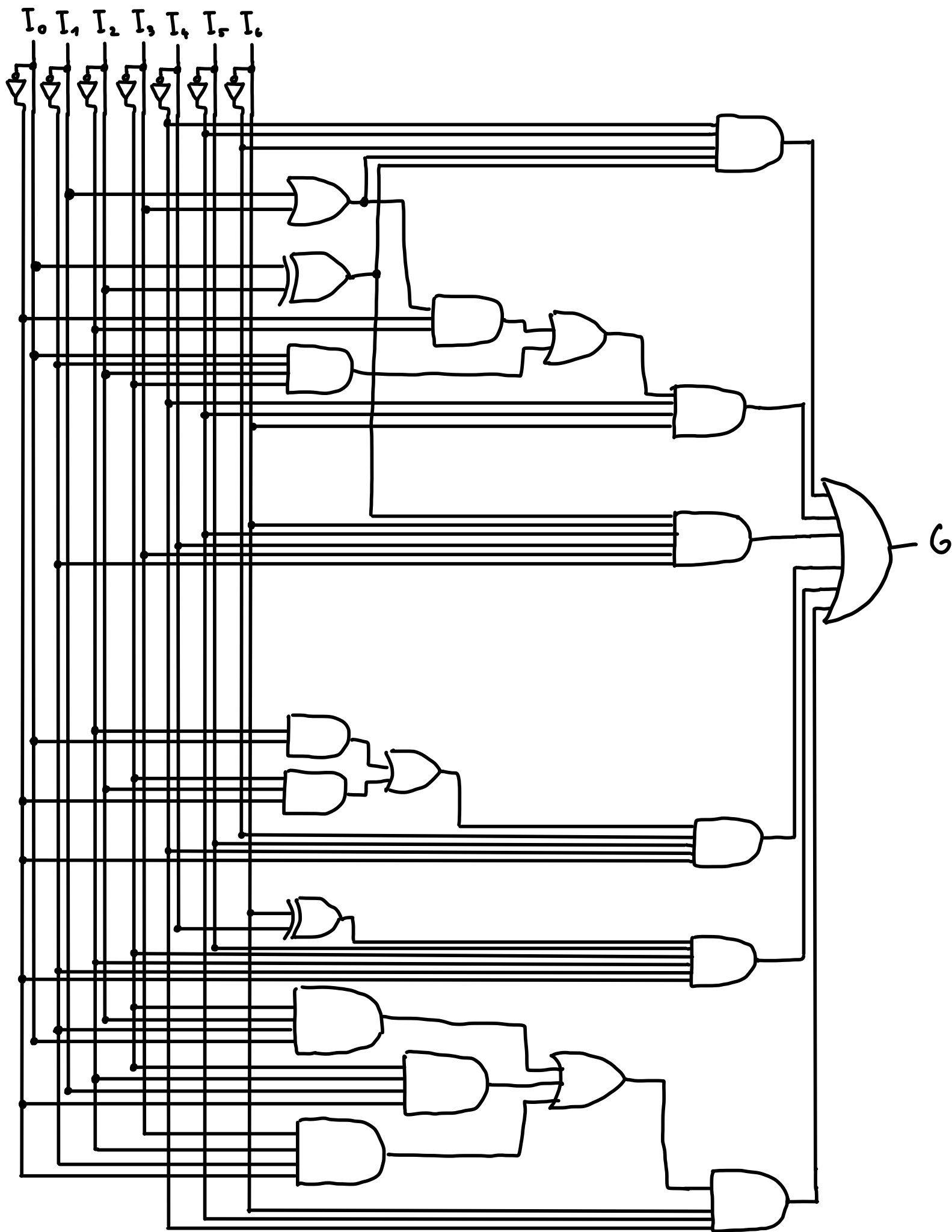

2

Flipping A can't cause a glitch because it appears in the formula only once.

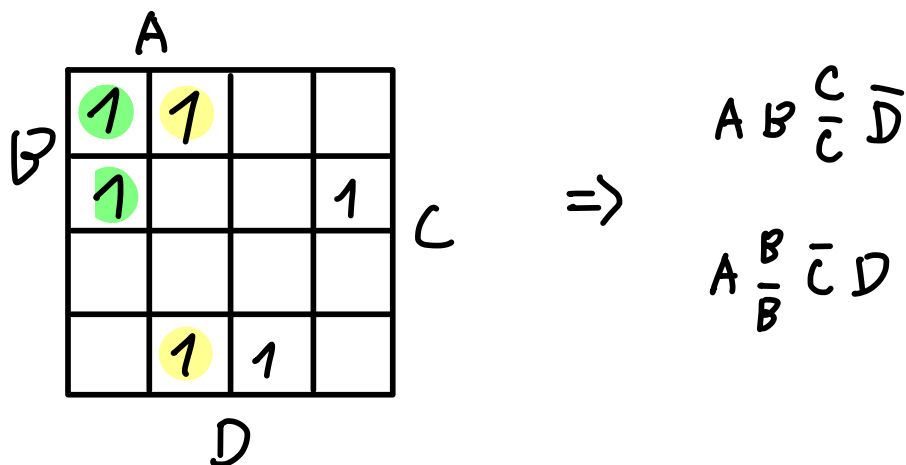Here's the Karnaugh map with pairs across terms that cause a glitch



Thus, the circuit glitches for $1100 \Leftrightarrow 1110$ and $1101 \Leftrightarrow 1001$.

We can fix this by adding a term for each of the pairs:

$$Y = (A \cdot B \cdot \bar{C}) + (B \cdot C \cdot \bar{D}) + (\bar{B} \cdot \bar{C} \cdot D) + (A \cdot \bar{B} \cdot \bar{D}) + (A \cdot \bar{C} \cdot D)$$

③

